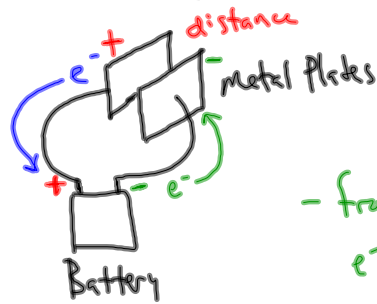


Capacitance:



- from movement of e^- , a ΔV is established bet. the plates.

- this creates an \vec{E} -field bet. the plates.

- Capacitance $\equiv \frac{\text{charge}}{\text{electric potential difference}}$

$$C \equiv \frac{Q}{\Delta V}$$

- Units: $1 \text{ Farad (F)} = 1 \frac{\text{C}}{\text{V}}$

- Three kinds:

- * 1. Parallel-plate
- 2. Cylindrical
- 3. Spherical

- For a parallel-plate capacitor:



$$A = wh$$

d is separation distance

$$\sigma = \frac{Q}{A}$$

Quick Derivation:

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

(lowercase epsilon naught permittivity of free space) (surface charge density)

$$\Delta V = E d = \frac{Q d}{\epsilon_0 A} \quad C = \frac{Q}{\Delta V} = \frac{Q}{\frac{Q d}{\epsilon_0 A}} = \frac{\epsilon_0 A}{d}$$

• Combining Capacitors:

- Components and Schematic representation:

Battery 


Wire 

Resistor 

Capacitor 

Switch  open
closed

- Wiring in parallel:

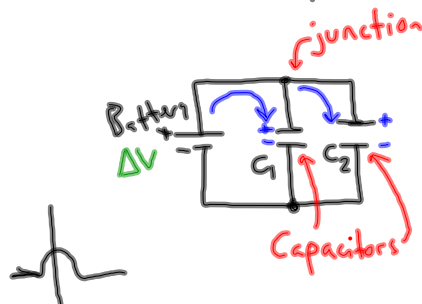


- technically, e^- go from $-$ to $+$.

- what we call current goes from $+$ to $-$.

(conventional current)

$$C_{\text{net}} = C_1 + C_2 + \dots$$

- Wiring in series:

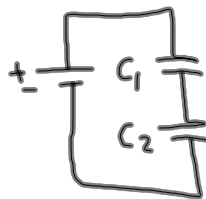

$$\frac{1}{C_{\text{net}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$